


# CPSC 359 – Digital Logic Tutorial #2

## Multiplexing

Andrew Kuipers




# Multiplexers

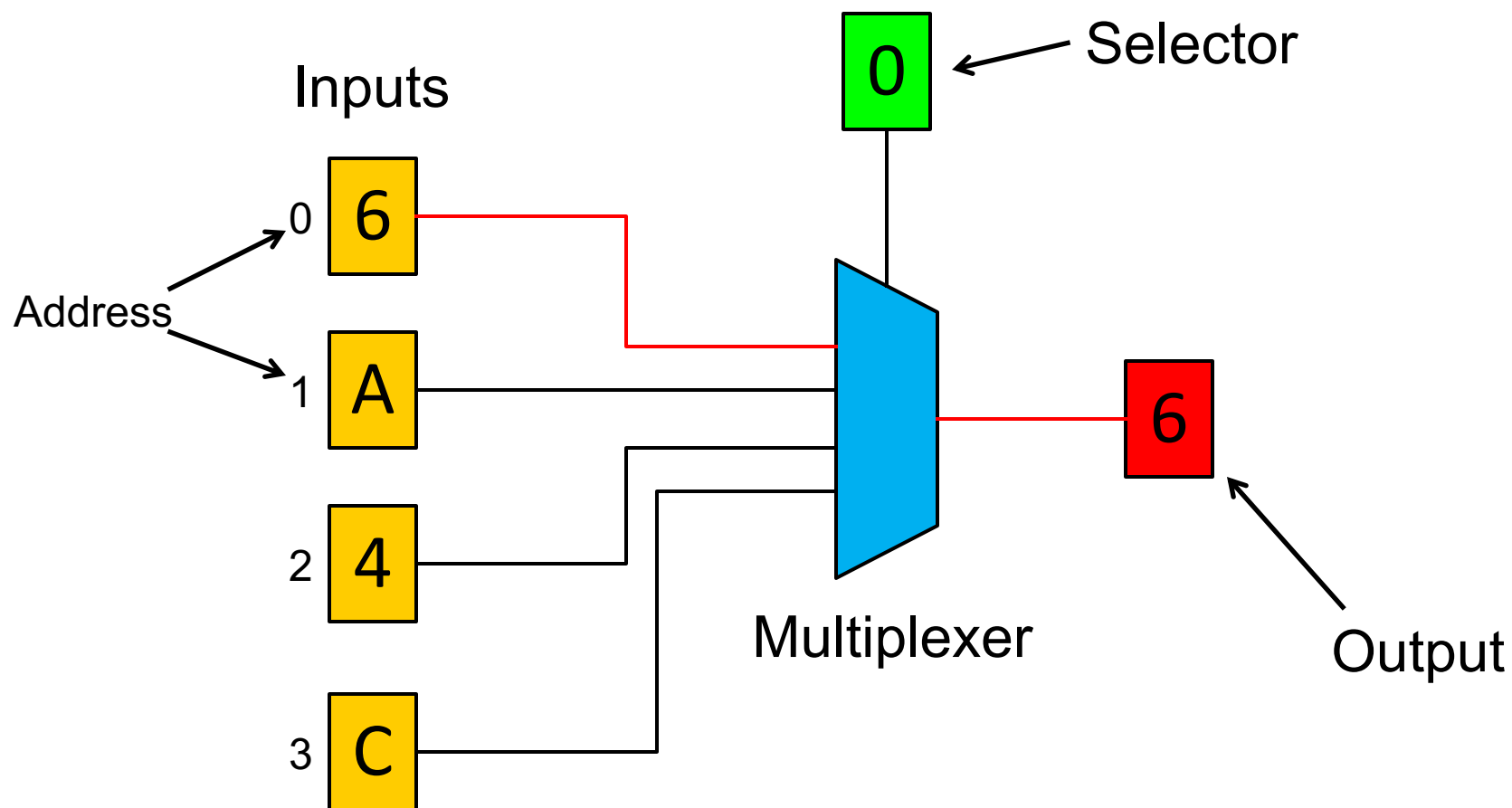




# Multiplexers

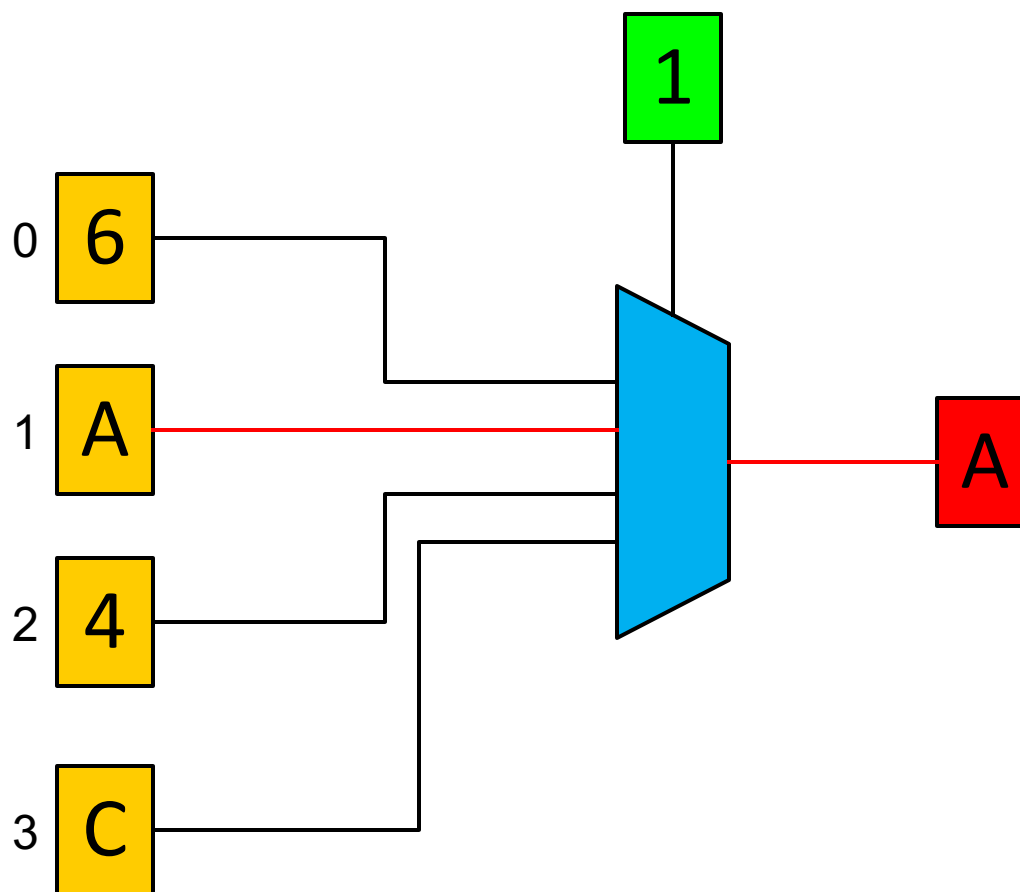




# Multiplexers

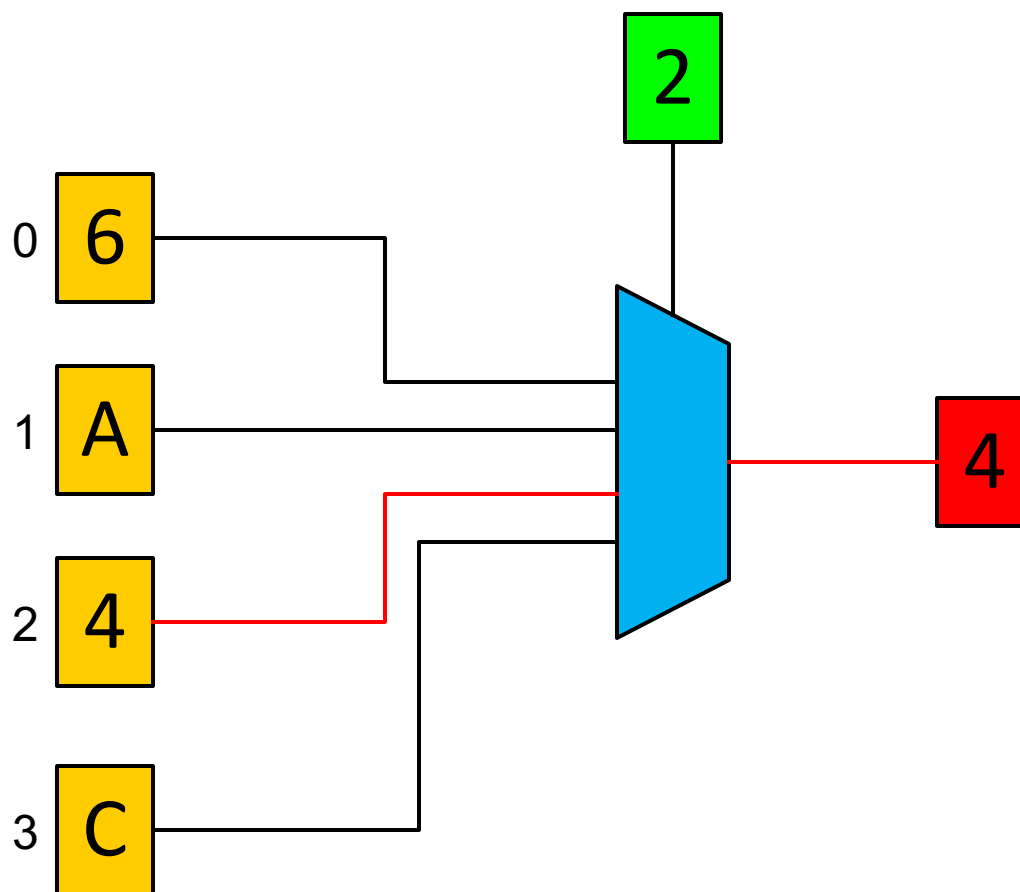




# Multiplexers

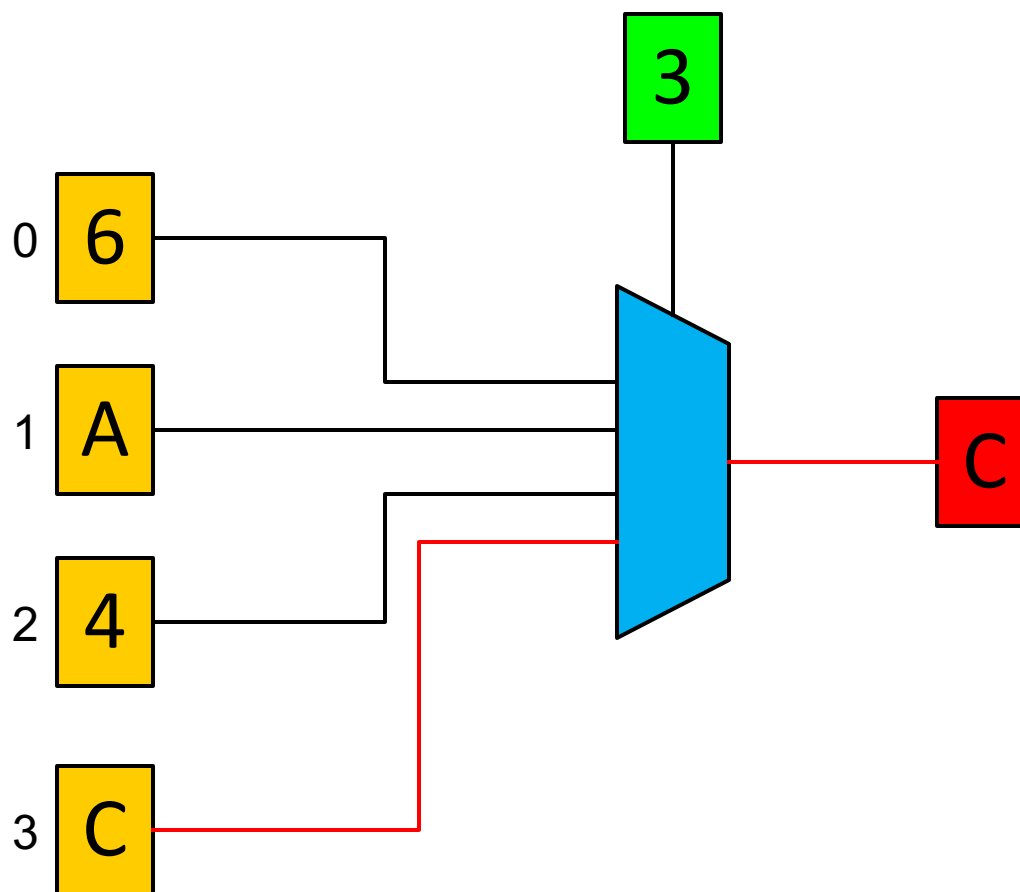
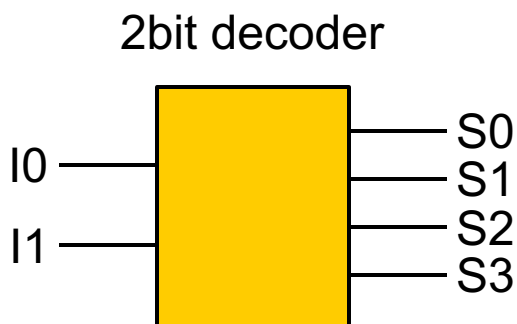
# Decode the Address


- First, we need to decode the address to select the line
  - Input:  $n$  bit address
  - Output:  $2^n$  selector lines



I1	I0	S0	S1	S2	S3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

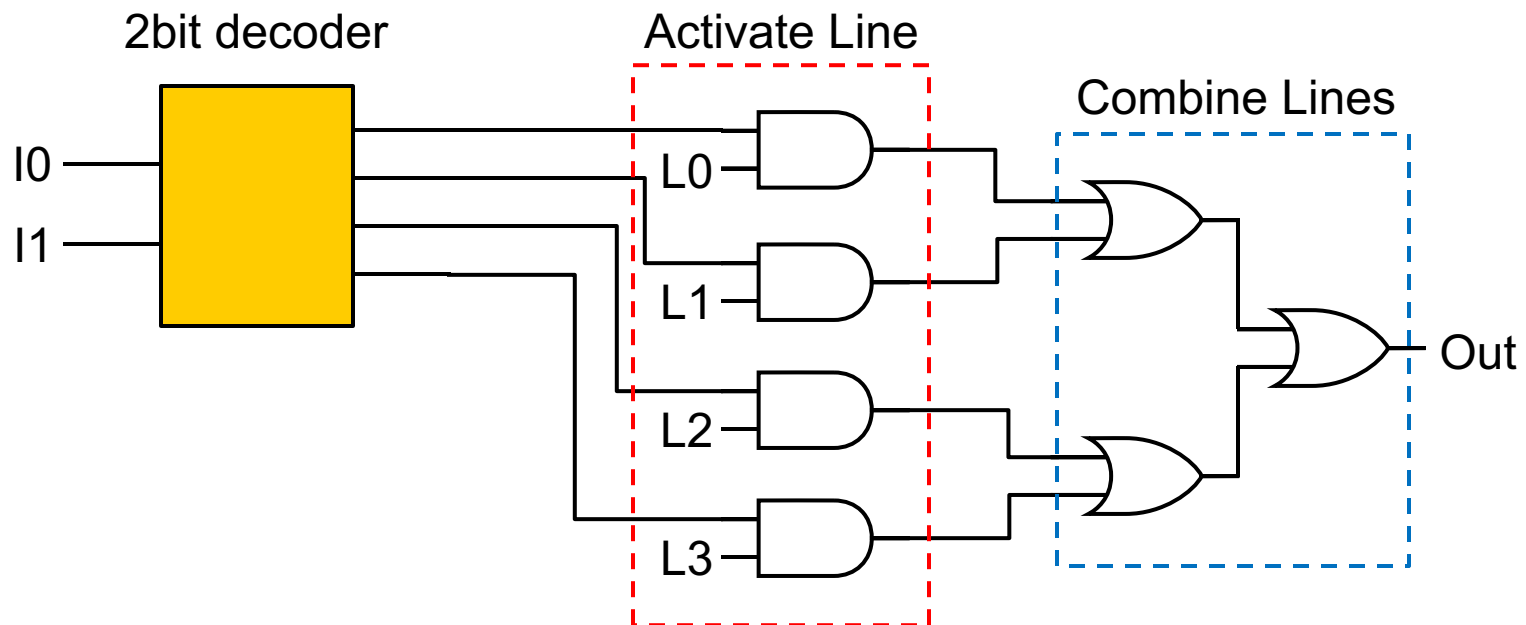
# Activate the Line

- Use the output of the decoder to activate the correct line



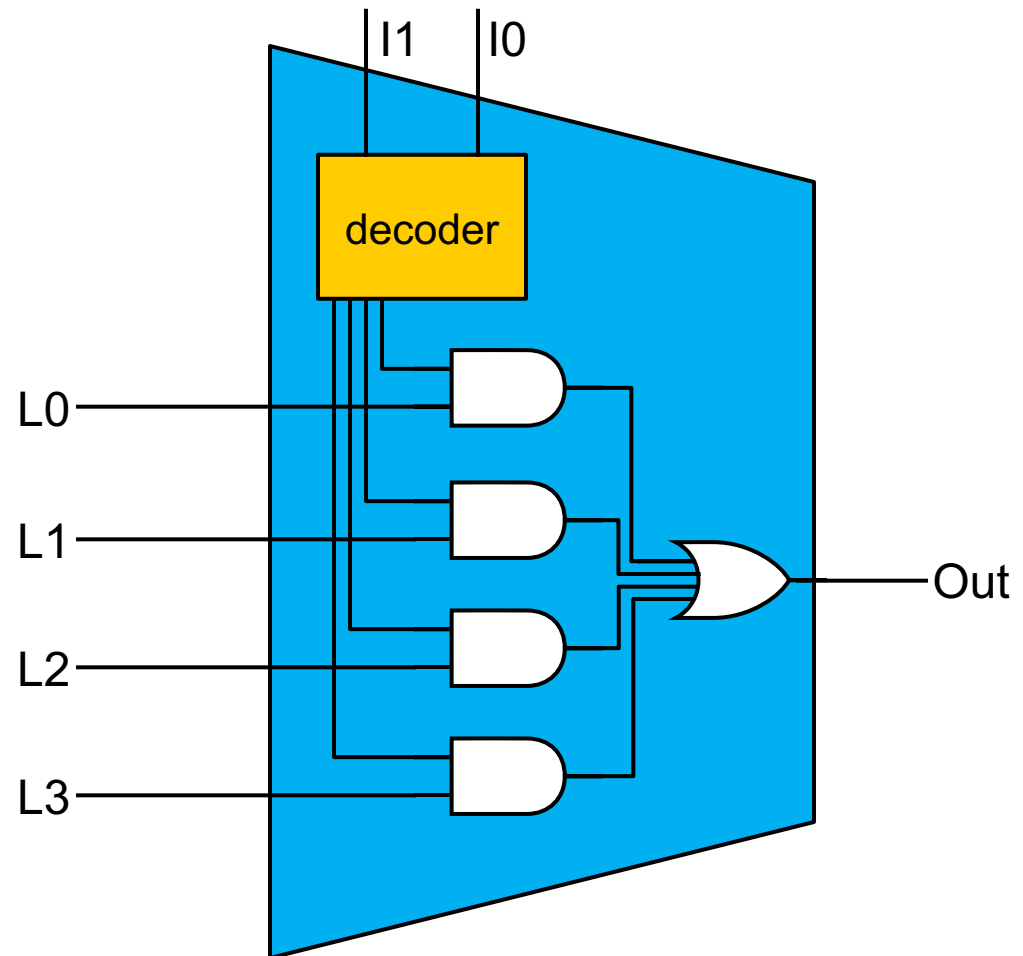
# Activate the Line

- 4 to 1 multiplexer
  - 2bit address space
- What we have:
  - Four 1bit inputs
  - One 1bit output
- What we want:
  - Four 4bit inputs
  - One 4bit output





# Exercise

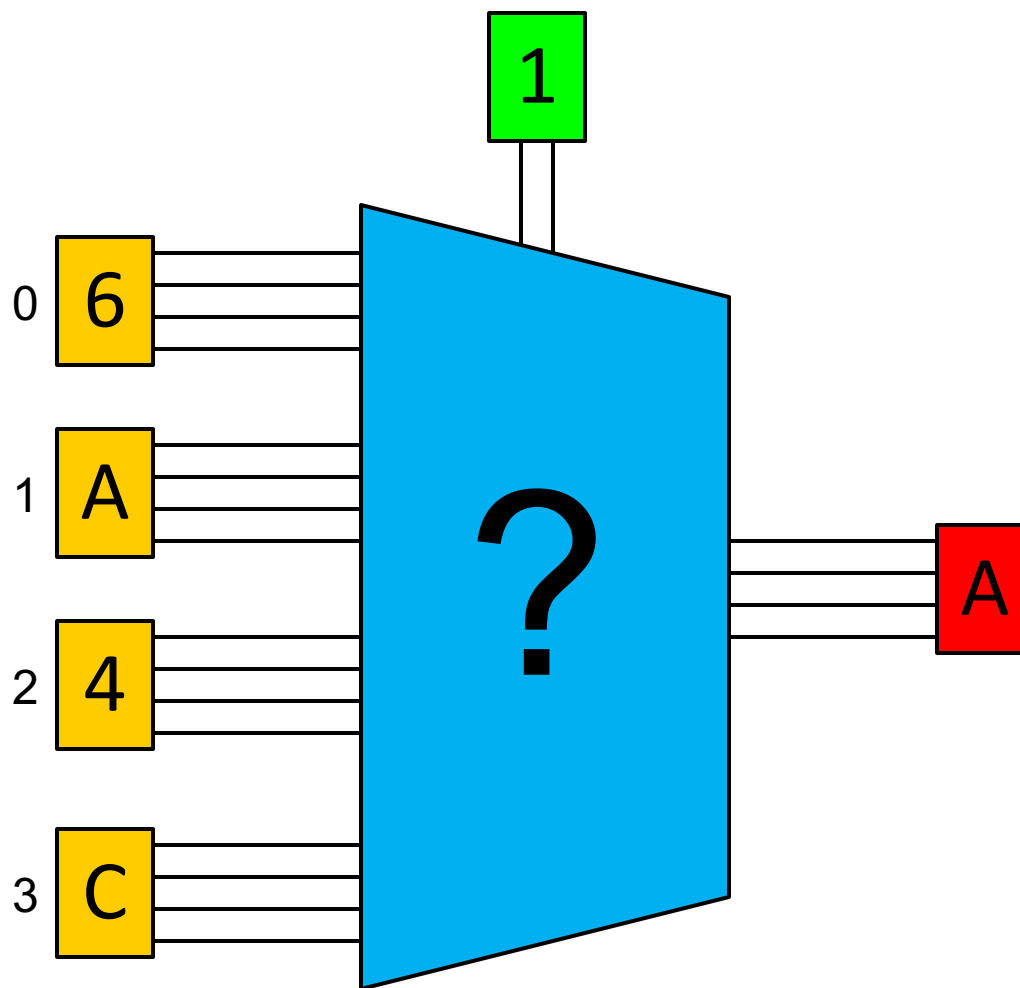

# Challenge Exercises

1. Combine the Multiplexer with the 4bit Full Adder
  - Use 4bit Full Adder circuit from lecture
  - Two 4bit 4-to-1 multiplexers to select each input to the adder
  
2. Create a 4bit 1-to-4 Demultiplexer
  - It's like a multiplexer, just in reverse!
  - One 2bit selector and one 4bit value input
  - Four 4bit value outputs