

CPSC 359 – Digital Logic Tutorial #3


Latches and Flip-Flops

Andrew Kuipers

Latches

Feedback and Latching


$$Q_t = S \vee Q_{t-1}$$

 

Latches

Feedback and Latching

$$Q_t = S \vee Q_{t-1}$$

 


t	S	Q
0	0	0
1		
2		

Latches

Feedback and Latching

$$Q_t = S \vee Q_{t-1}$$

 


t	S	Q
0	0	0
1	1	
2		

Latches

Feedback and Latching

$$Q_t = S \vee Q_{t-1}$$

 


t	S	Q
0	0	0
1	1	1
2		

Latches

Feedback and Latching

$$Q_t = S \vee Q_{t-1}$$

 


t	S	Q
0	0	0
1	1	1
2	0	

Latches

Feedback and Latching

$$Q_t = S \vee Q_{t-1}$$

 


t	S	Q
0	0	0
1	1	1
2	0	1

Latches

Feedback and Latching

$$Q_t = S \vee Q_{t-1}$$

 


t	S	Q
0	0	0
1	1	1
2	0	1

How can we turn off this line?

Latches

Feedback and Latching


$$Q_t = S \vee (Q_{t-1} \wedge \neg R)$$

 

Latches

Feedback and Latching

$$Q_t = S \vee (Q_{t-1} \wedge \neg R)$$

 


t	S	R	Q
0	0	0	0
1			
2			
3			
4			

Latches

Feedback and Latching

$$Q_t = S \vee (Q_{t-1} \wedge \neg R)$$

 


t	S	R	Q
0	0	0	0
1	1	0	
2			
3			
4			

Latches

Feedback and Latching

$$Q_t = S \vee (Q_{t-1} \wedge \neg R)$$

 


t	S	R	Q
0	0	0	0
1	1	0	1
2			
3			
4			

Latches

Feedback and Latching

$$Q_t = S \vee (Q_{t-1} \wedge \neg R)$$

 


t	S	R	Q
0	0	0	0
1	1	0	1
2			
3			
4			

Latches

Feedback and Latching

$$Q_t = S \vee (Q_{t-1} \wedge \neg R)$$

 


t	S	R	Q
0	0	0	0
1	1	0	1
2	0	0	
3			
4			

Latches

Feedback and Latching

$$Q_t = S \vee (Q_{t-1} \wedge \neg R)$$

 


t	S	R	Q
0	0	0	0
1	1	0	1
2	0	0	1
3			
4			

Latches

Feedback and Latching

$$Q_t = S \vee (Q_{t-1} \wedge \neg R)$$

 


t	S	R	Q
0	0	0	0
1	1	0	1
2	0	0	1
3	0	1	
4			

Latches

Feedback and Latching

$$Q_t = S \vee (Q_{t-1} \wedge \neg R)$$

 


t	S	R	Q
0	0	0	0
1	1	0	1
2	0	0	1
3	0	1	
4			

Latches

Feedback and Latching

$$Q_t = S \vee (Q_{t-1} \wedge \neg R)$$

 


t	S	R	Q
0	0	0	0
1	1	0	1
2	0	0	1
3	0	1	
4			

Latches

Feedback and Latching

$$Q_t = S \vee (Q_{t-1} \wedge \neg R)$$

 


t	S	R	Q
0	0	0	0
1	1	0	1
2	0	0	1
3	0	1	0
4			

Latches

Feedback and Latching

$$Q_t = S \vee (Q_{t-1} \wedge \neg R)$$

 


t	S	R	Q
0	0	0	0
1	1	0	1
2	0	0	1
3	0	1	0
4	0	0	

Latches

Feedback and Latching

$$Q_t = S \vee (Q_{t-1} \wedge \neg R)$$

 


t	S	R	Q
0	0	0	0
1	1	0	1
2	0	0	1
3	0	1	0
4	0	0	

Latches

Feedback and Latching

$$Q_t = S \vee (Q_{t-1} \wedge \neg R)$$

 


t	S	R	Q
0	0	0	0
1	1	0	1
2	0	0	1
3	0	1	0
4	0	0	0

Latches

SR Latch

 
$$Q = \neg(R \vee \neg Q)$$
$$\neg Q = \neg(S \vee Q)$$



Latches

Gated SR Latch

 
$$Q = \neg((R \wedge E) \vee \neg Q)$$
$$\neg Q = \neg((S \wedge E) \vee Q)$$



Latches

Gated D Latch
 
$$Q = \neg((\neg D \wedge E) \vee \neg Q)$$
$$\neg Q = \neg((D \wedge E) \vee Q)$$




Latches

Exercise

1. Create a new circuit with 4 D Latches (as imported modules)
2. Use an Input component to select which D Latch is enabled
 - Only use the two least significant bits
 - Can use the 2bit Decoder circuit from previous tutorial
3. Selectively set and clear different D Latches


Flip-Flops

Level Trigger vs Edge Trigger

 

Flip-Flops

Level Trigger vs Edge Trigger

 


Flip-Flops

Level Trigger vs Edge Trigger


Flip-Flops

Level Trigger vs Edge Trigger

 

Flip-Flops

Level Trigger vs Edge Trigger

 


Only change on rising edge of E

Flip-Flops


Level Trigger vs Edge Trigger

Positive Edge Trigger

 

Only change on rising edge of E


Negative Edge Trigger

 

Flip-Flops


Level Trigger vs Edge Trigger

Positive Edge Trigger

 

Only change on rising edge of E

Negative Edge Trigger

 

Only change on falling edge of E




Flip-Flops

Master-Slave D Flip-Flop

Flip-Flops

Master-Slave D Flip-Flop


Positive Edge Triggered

 


Flip-Flops

Master-Slave D Flip-Flop

Positive Edge Triggered

 


Negative Edge Triggered

 

Flip-Flops

Example – Shift Register

 

Data is right-shifted through the register
on each triggering edge (neg. or pos.)

Flip-Flops

Exercise

1. Create a 4bit register using D Flip-Flops
 - 4 input “load” lines
 - 4 output “value” lines
 - 1 load enable line (clock line)
2. Create a new circuit, add 4 of these registers as modules
3. Combine with 2bit Decoder to select which register is enabled
4. Load different values into these registers using an Input component

Flip-Flops

Challenge

Create a simple adding machine:

- Select input values from two of four 4bit registers
 - Need to be able to load the registers with values as well
- Store sum of input values in any of the four registers
 - Monitor values (inputs, output) for operation