

# CPSC 359 – Digital Logic Tutorial #1


## Basic Gates

Andrew Kuipers

# Basic Gates

## AND


$$C = A \wedge B$$

 

A	B	$A \wedge B$
0	0	0
0	1	0
1	0	0
1	1	1

## OR


$$C = A \vee B$$

 

A	B	$A \vee B$
0	0	0
0	1	1
1	0	1
1	1	1

## NOT


$$B = \neg A$$

 

A	$\neg A$
0	1
1	0
 
# Example


$$D = (\neg A \vee B) \wedge \neg(B \wedge \neg C)$$



A	B	C	$(\neg A \vee B) \wedge \neg(B \wedge \neg C)$					
0	0	0						
0	0	1						
0	1	0						
0	1	1						
1	0	0						
1	0	1						
1	1	0						
1	1	1						
 
# Example


$$D = (\neg A \vee B) \wedge \neg(B \wedge \neg C)$$



A	B	C	$(\neg A \vee B) \wedge \neg(B \wedge \neg C)$				
0	0	0					1
0	0	1					0
0	1	0					1
0	1	1					0
1	0	0					1
1	0	1					0
1	1	0					1
1	1	1					0
 
# Example


$$D = (\neg A \vee B) \wedge \neg(B \wedge \neg C)$$



A	B	C	$(\neg A \vee B) \wedge \neg(B \wedge \neg C)$					
0	0	0					0	1
0	0	1					0	0
0	1	0					1	1
0	1	1					0	0
1	0	0					0	1
1	0	1					0	0
1	1	0					1	1
1	1	1					0	0
 
# Example


$$D = (\neg A \vee B) \wedge \neg(B \wedge \neg C)$$



A	B	C	$(\neg A \vee B) \wedge \neg(B \wedge \neg C)$					
0	0	0				1	0	1
0	0	1				1	0	0
0	1	0				0	1	1
0	1	1				1	0	0
1	0	0				1	0	1
1	0	1				1	0	0
1	1	0				0	1	1
1	1	1				1	0	0
 
# Example


$$D = (\neg A \vee B) \wedge \neg(B \wedge \neg C)$$



A	B	C	$(\neg A \vee B) \wedge \neg(B \wedge \neg C)$					
0	0	0	1			1	0	1
0	0	1	1			1	0	0
0	1	0	1			0	1	1
0	1	1	1			1	0	0
1	0	0	0			1	0	1
1	0	1	0			1	0	0
1	1	0	0			0	1	1
1	1	1	0			1	0	0
 
# Example

$$D = (\neg A \vee B) \wedge \neg(B \wedge \neg C)$$




A	B	C	$(\neg A \vee B) \wedge \neg(B \wedge \neg C)$					
0	0	0	1	1		1	0	1
0	0	1	1	1		1	0	0
0	1	0	1	1		0	1	1
0	1	1	1	1		1	0	0
1	0	0	0	0		1	0	1
1	0	1	0	0		1	0	0
1	1	0	0	1		0	1	1
1	1	1	0	1		1	0	0


 
# Example


$$D = (\neg A \vee B) \wedge \neg(B \wedge \neg C)$$



A	B	C	$(\neg A \vee B) \wedge \neg(B \wedge \neg C)$					
0	0	0	1	1	1	1	0	1
0	0	1	1	1	1	1	0	0
0	1	0	1	1	0	0	1	1
0	1	1	1	1	1	1	0	0
1	0	0	0	0	0	1	0	1
1	0	1	0	0	0	1	0	0
1	1	0	0	1	0	0	1	1
1	1	1	0	1	1	1	0	0

# Exercise

1. Translate to a logical formula:

 

2. Create a circuit for the logical formula:


$$D = \neg(A \wedge \neg B) \wedge (C \vee \neg A \vee B)$$

---

# Other Gates

## XOR


$$C = A \oplus B$$

 

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

## NOR


$$C = \neg(A \vee B)$$

 

A	B	$\neg(A \vee B)$
0	0	1
0	1	0
1	0	0
1	1	0

## NAND

$$C = \neg(A \wedge B)$$

 

A	B	$\neg(A \wedge B)$
0	0	1
0	1	1
1	0	1
1	1	0

# Transforming Circuits

## De Morgan's Laws

$$\neg(A \wedge B) \Leftrightarrow \neg A \vee \neg B$$

$$\neg(A \vee B) \Leftrightarrow \neg A \wedge \neg B$$

**So:**  $A \wedge B \Leftrightarrow \neg(\neg A \vee \neg B)$  *and*  $A \vee B \Leftrightarrow \neg(\neg A \wedge \neg B)$



**Therefore:** Just need  $\{ \wedge, \neg \}$  or  $\{ \vee, \neg \}$  for any circuit

---

# Transforming Circuits

 
 
**NOR can make a NOT gate:**

$$\neg A \Leftrightarrow \neg A \wedge \neg A \Leftrightarrow \neg(A \vee A)$$



  **NOR can make an OR gate:**

$$A \vee B \Leftrightarrow \neg(\neg(A \vee B))$$




**So:** NOR gates alone can be used to make any circuit

\* can NAND gates do the same thing?
 
# Exercise

Translate into a circuit using only NOR gates:



\* Can you optimize the number of gates used?