

Digital Logic

II. *Combinational Circuits*

Jalal Kawash

A series of horizontal lines of varying lengths and colors (teal, light blue, and white) extending from the right side of the slide.

Outline

1. Types of Circuits
2. Basic Combinational Circuits
 - a. Adders
 - b. Decoders
3. ALUs
4. More Combinational Circuits
 - a. Multiplexers
 - b. Multipliers
 - c. Comparators

Digital Logic 2

Combinational Circuits

Section 1

Types of Digital Circuits

Digital Logic II

Combinational Circuits


Section 1 Objective

At the end of this section you will

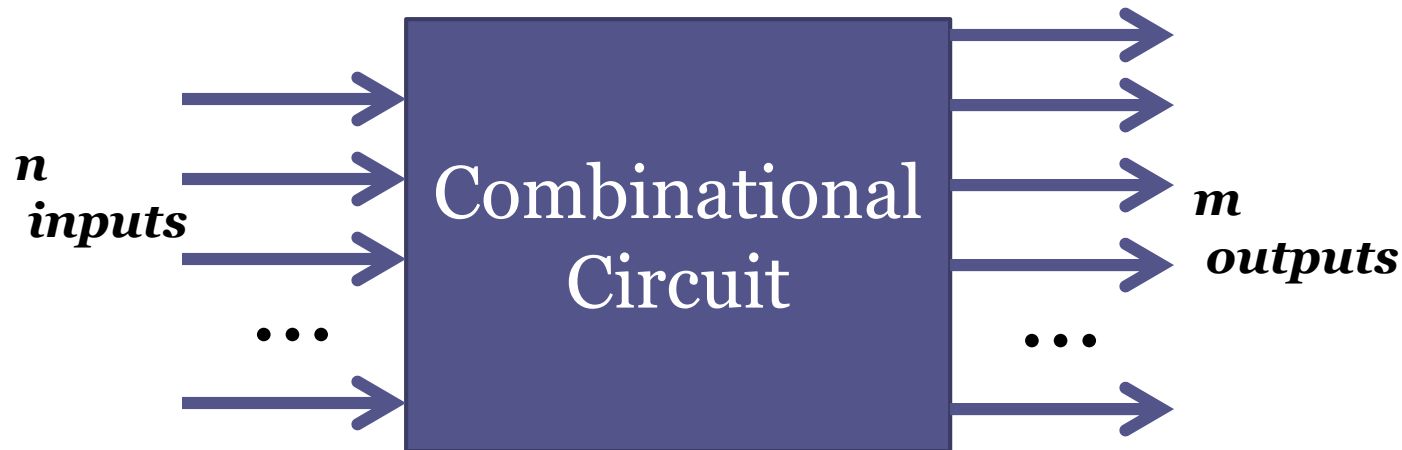1. Understand the difference between combinational and sequential circuits

Combinational Circuits


- A combinational circuit is a logic circuit whose output is solely determined by the inputs



Sequential Circuits

- Unlike a combinational circuit, the output of a sequential circuit at time t can affect the circuits output at time $t+1$

Sequential Circuits

 

Digital Logic II

Combinational Circuits

Section 2

Basic Circuits

Section 2 Objectives

At the end of this section you will

1. Be able to build half-adder (HA) circuits
2. Understand HA limitations
3. Be able to build full-adder (FA) circuits
4. Chain combinational circuits
5. Be able to build decoders
6. Understand how to use decoders as “switches” to build mult-function circuits

Half Adder (HA)


- Input: two bits, x and y
- Output: $x + y$

x	y	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

HA Circuit

x	y	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 - $\text{Sum} = x'y + y'x = x \oplus y$
- $\text{Carry} = xy$



Source: DL2.circ (HA)


Limitation of a HA

- Can we build an adder for 2-bit numbers from the 1-bit HAs?



Limitation of a HA

 - Can we build an adder for 2-bit numbers from the 1-bit HAs? Does not work if $x_0 + y_0$ produce a carry!



Need an adder with 3 inputs
HA has only 2!

Full Adder (FA)

- Input: three bits, x , y , and z
- Output: $x + y + z$

x	y	z	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Full Adder - BSP for Carry

<i>x</i>	<i>y</i>	<i>z</i>	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$x'yz$

$xy'z$

xyz'

xyz

Carry Function

- $Carry = x'yz + xy'z + xyz' + xyz$

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

- $Carry = x(y'z + yz') + yz$
- $Carry = x(y \oplus z) + yz$

Full Adder - BSP for Sum

<i>x</i>	<i>y</i>	<i>z</i>	Sum	Carry	
0	0	0	0	0	
0	0	1	1	0	$x'y'z$
0	1	0	1	0	$x'yz'$
0	1	1	0	1	
1	0	0	1	0	$xy'z'$
1	0	1	0	1	
1	1	0	0	1	
1	1	1	1	1	xyz

Sum Function

- $\text{Sum} = x'y'z + x'yz' + xy'z' + xyz$
- ***Map is useless!!***

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

Sum Function

- Observation: $(a \oplus b)' = a'b' + ab$

- *Proof:*

- $(a \oplus b)' = (a'b + b'a)'$

xor definition

- $(a \oplus b)' = (a'b)'(b'a)'$

DeMorgan's law

- $(a \oplus b)' = (a'' + b')(b'' + a')$

DeMorgna's law

- $(a \oplus b)' = (a + b')(b + a')$

Double negation

- $(a \oplus b)' = ab + a'a + b'b + a'b'$

Distribution

- $(a \oplus b)' = ab + a'b'$


$xx' = 0, x+0=x$

Sum Function

- $Sum = x'y'z + x'yz' + xy'z' + xyz$
- $Sum = x'(y'z + yz') + x(y'z' + yz)$
- $Sum = x'(y \oplus z) + x(y \oplus z)'$
- $Sum = x \oplus y \oplus z$
 - $Let\ a = (y \oplus z),\ Sum = x'a + xa' = x \oplus a$

FA Circuit

 
- $Sum = x \oplus y \oplus z$
- $Carry = x(y \oplus z) + yz$



Chaining FAs (2-bit number FA)




Add x_1x_0 to y_1y_0

 

Result is $C_1S_1S_0$




4-bit Adder

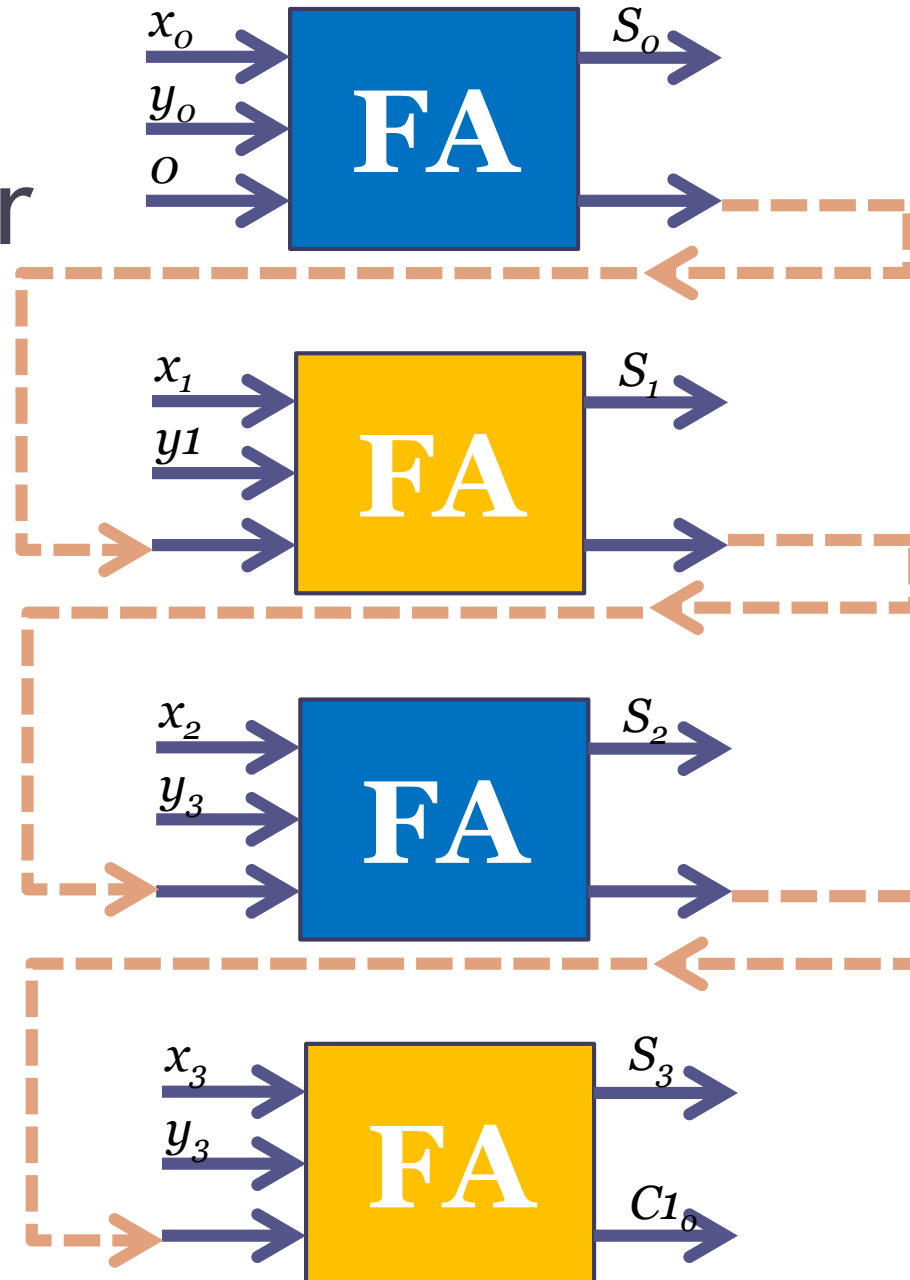

Chaining

 - Chaining is an easy way to build “higher-order” circuits from “lower-order” ones
- However, it is not the best
- The longer the chain the slower the circuit





Full Subtractor

- Can be built from a FA
- $x - y = x (y \oplus 1) + 1$
- *Why?*



Decoders

- A decoder is a combinational circuit such that
 - It has n inputs
 - It has 2^n outputs
 - For each input a unique associated output line carries 1
 - All other lines carry 0
 - Let b_n be the binary number corresponding to the input bits
 - If the input is b_n , then line b_n is set (carries 1)


2-4 Decoder

  

2-4 Decoder

  


2-4 Decoder

 

Multi-Function Circuits

- Hardware runs all the time
- A multi-function circuit will compute all of its functions
- A decoder is used to “filter out” the functions that are not required


4-Function Circuit

 

2-4 Decoder (Truth Table)

x	y	F_0	F_1	F_2	F_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

2-4 Decoder (Circuit)

 

Source: DL2 (2-4 Decoder)

3-8 Decoder

- Exercise

Digital Logic II

Combinational Circuits

Section 3

A Simple ALU

Digital Logic II

Combinational Circuits

Section 3 Objectives


At the end of this section you will

1. Build a simple 1-bit ALU
2. Use chaining to build higher order ALU


Bit Slice


- A bit slice is a 1-bit ALU
- We will use chaining to create a larger ALU
- ALU can do
 - And
 - Or
 - Not
 - Addition
 - Only

Logic Unit

 

Source: DL2 (Logic Unit)

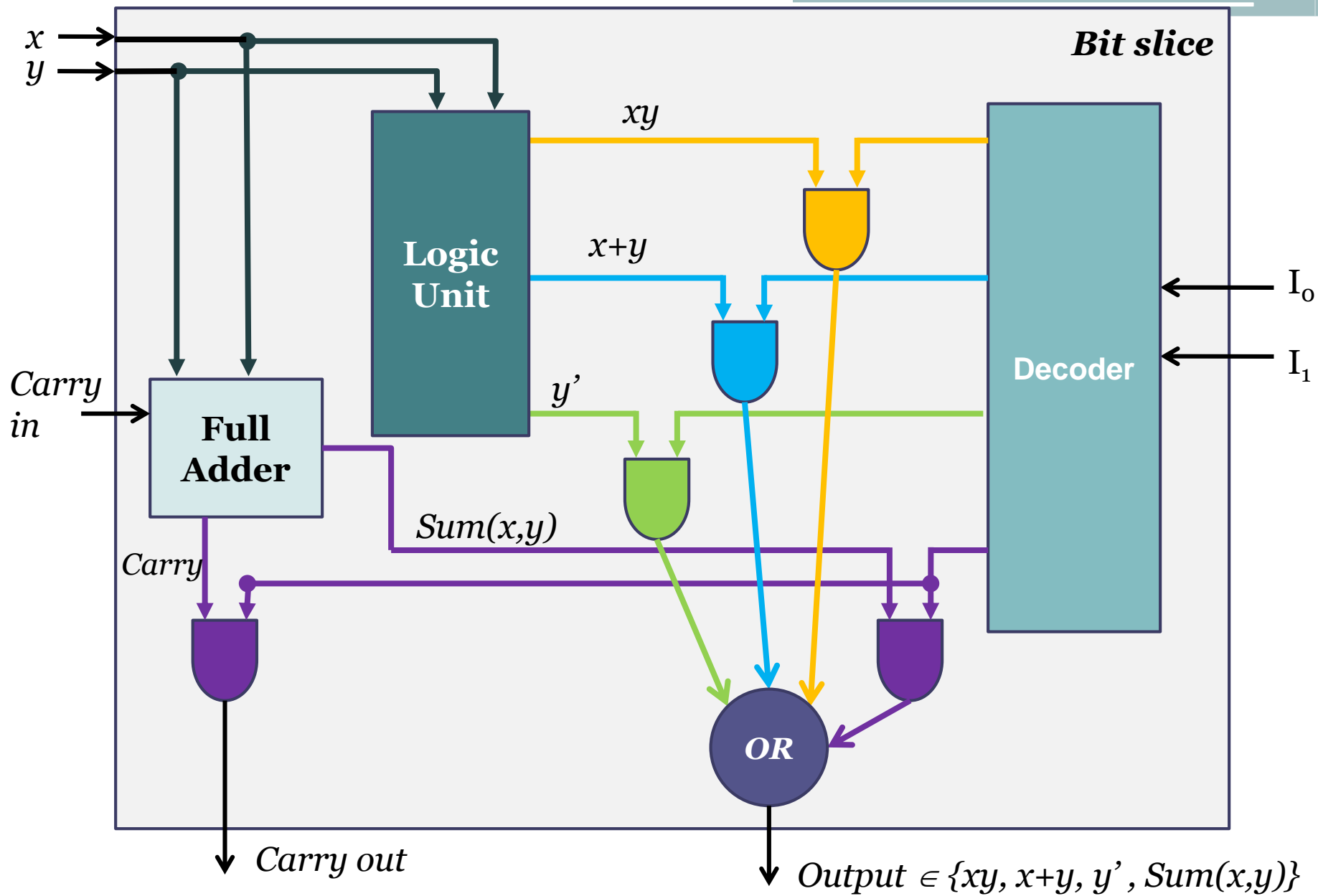


 

Bit slice demo

Source: DL2.circ (Bit Slice)

4-bit ALU (by chaining)

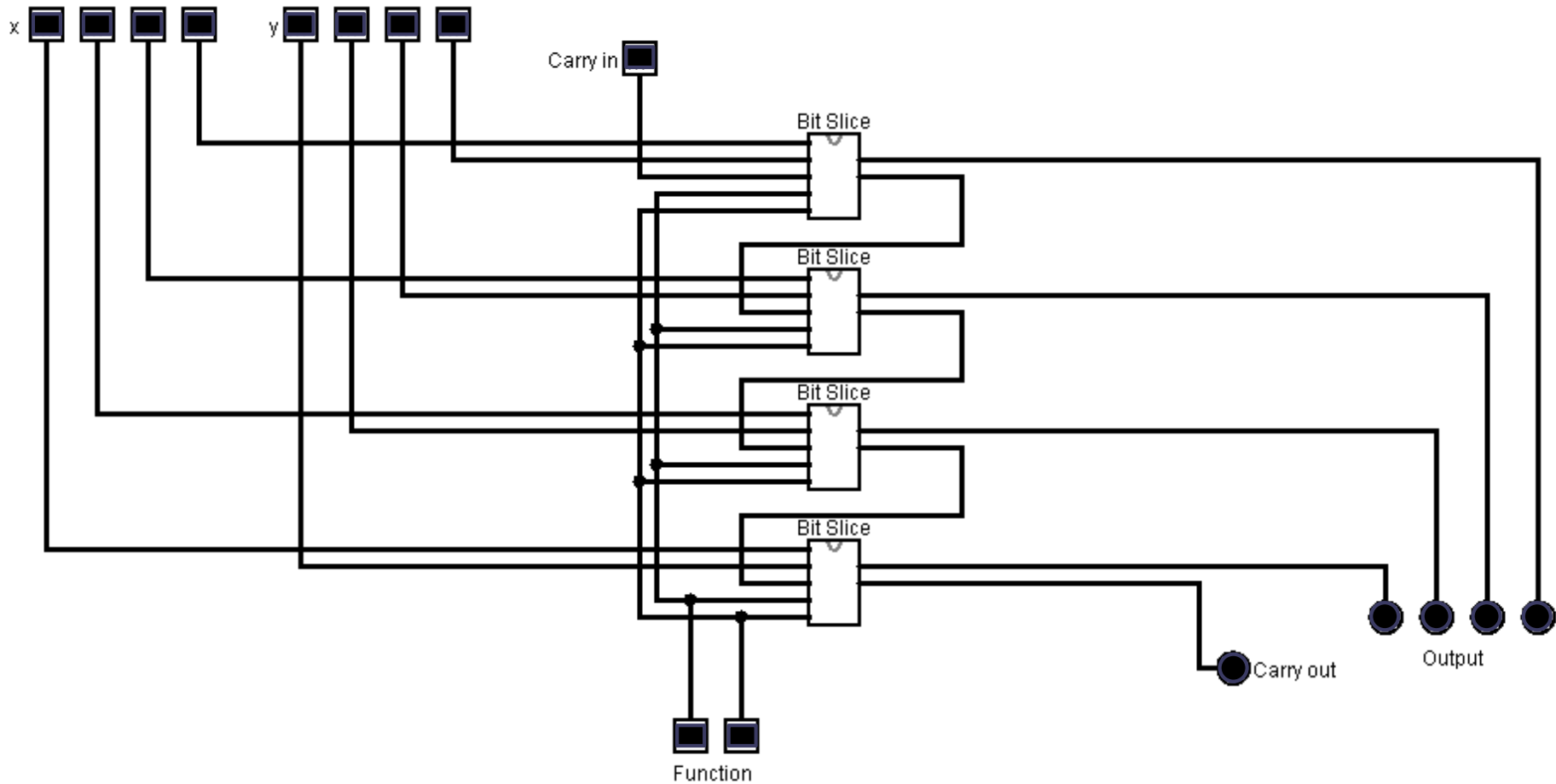

Source: DL2 (4-bit ALUS)

Digital Logic II

Combinational Circuits

Section 4

More Combinational Circuits

Digital Logic II


Combinational Circuits

Section 4 Objective

At the end of this section you will


1. Gain more practice with combinational circuits

Multiplexers

 


- If $S = 0$, $X = I_0$
- If $S = 1$, $X = I_1$

4-Input Multiplexer

 

Source: D2l.circ (4-input Multiplexer)

Shifters

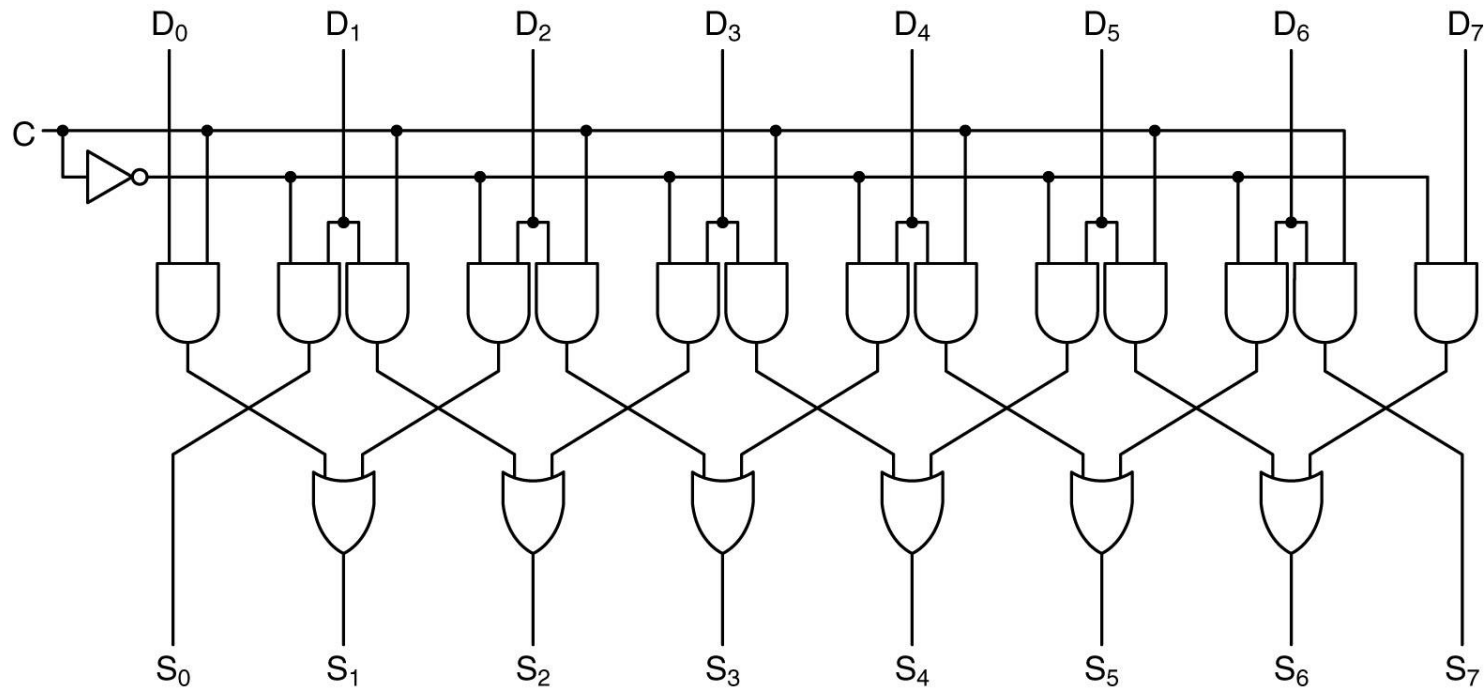


1-bit left/right shifter.
 $C = 0$ for left 1 for right

Left Shift

C = 0

$D_0 D_1 D_2 D_3 D_4 D_5 D_6 D_7$

$D_1 D_2 D_3 D_4 D_5 D_6 D_7 0$

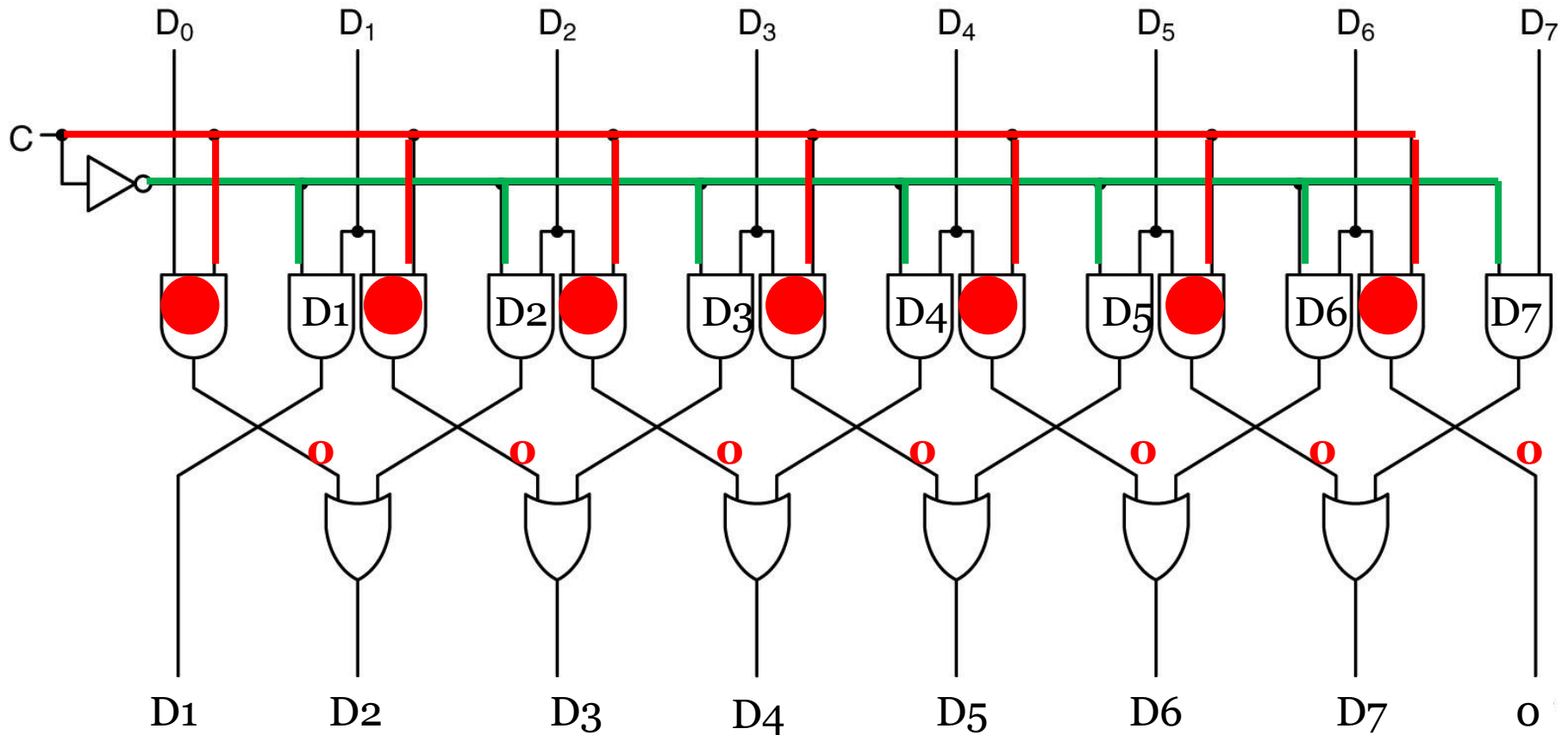


Right Shift

$C = 1$


$D_0 D_1 D_2 D_3 D_4 D_5 D_6 D_7$

$0 D_0 D_1 D_2 D_3 D_4 D_5 D_6$

 

Comparators

 - Two bits can be compared with a XOR gate
- Two numbers can be compared bit-wise



Magnitude Comparator

- Challenge yourself with designing a circuit that inputs 2-bit binary numbers A & B
- It has 3 outputs:
 - First output is 1, iff the numbers are equal
 - Second is 1, iff $A < B$
 - Third is 1, iff $A > B$
- Repeat for 4 bit numbers

Multipliers

- Multiplication can be done by addition
- To multiply X and Y , add Y to itself X times; or add X to itself Y times
- Challenge yourself to build a “direct” multiplier
 - i.e., do not use the method described above
 - Hint: fix the size of your inputs; e.g., multiply 2-bit by a 3-bit number

Self-Test Quiz

- Challenge yourself to build a “direct” multiplier that multiplies 2-bit by a 3-bit number