

CPSC 359 – Fall 2019

Assignment 2: A Sequential Circuit for Slow Integer Division

due: 0900h 21-Oct-2019

Background

In this assignment, you will *program* a sequential circuit to implement an algorithm for integer division. While the circuit is very specific to this task, it is a simplification of many of the elements of a CPU. Your *program* will be equivalent to the *microcode* in a CPU that establishes the machine-code/assembly language for the device.

Objective

Design and implement a sequential logic circuit that divides two unsigned 32-bit integers.

Details

Algorithm 1 shows how to divide two unsigned integers using binary arithmetic. I have provided you with a *Logisim* template to implement this algorithm (Figure 1).

Algorithm 1 Algorithm to divide two unsigned integers (the slow way).

Require: unsigned operands a and b

Ensure: $x = a/b$, $a = a \bmod b$

```
1:  $x \leftarrow 0$ 
2: while  $a \geq b$  do
3:    $x \leftarrow x + 1$ 
4:    $a \leftarrow a - b$ 
5: end while
```

There are three 32-bit registers in the template. These correspond to the values of a , b and x in Algorithm 1. Two of the registers have 2-into-1 multiplexers connected to the D input. When setting one of these values, the state of the multiplexer selects the source of the new value loaded into the register on a low-to-high clock transition. Table 1 summarizes the loaded values for the three registers. The template has additional components to compute values for $a < b$, $x + 1$, and $a - b$.

The template has a start button to initiate the algorithm. Alternatively, if you are stepping through the states to debug your circuit, there is an input pin that you can use to statically set the value of the start signal (make stepping a bit easier).

register	sel = 0	sel = 1
a	$a \leftarrow \text{first operand}$	$a \leftarrow a - b$
b	$b \leftarrow \text{second operand}$	
x	$x \leftarrow 0$	$x \leftarrow x + 1$

Table 1: Source values for register loads for given multiplexer select (sel) values.

Note, while you may use discrete logic gates to implement the combinational logic required, you will find it easier to use a read-only memory (ROM) as described in class.

Hints

1. Make sure you have an idle state. That way your machine can sit in constant state while you set inputs or read outputs.
2. A *start* signal can be used to initiate the computation.
3. The registers load when their clock signal goes high. It is important that the multiplex select bit be correct and stable when that happens. One way to do this is to set the select bit in the previous state, and maintain its value in the state that brings the *load* signal high.
4. I wrote a short Python program to help me with the ROM programming. It can save you a lot of time.

Evaluation

1	Identification of input/output/state variables.	2pts
2	Finite state machine - does task correctly.	6pts
3	Design of combinational logic/ROM programming.	5pts
4	Logisim implementation - runs correctly.	5pts
5	Logisim implementation - inputs/outputs labelled.	2pts
Total		20pts

There is no team work. Each student should submit their own solution.

Late work

After the deadline and up to 24hrs late: -5pts. After 24hrs and up to 48hrs late: -10pts. Over 48hrs late: -20pts, i.e., no assignment will be accepted beyond 48hrs after the deadline.

Plagiarism

Work must be the sole work of the individual submitting the work.

You may find that the design task for this assignment is similar to other well-known circuits. Nevertheless, you should go through the design process yourself, and submit your own work. If you do borrow from other sources, cite the source and clearly indicate what you have borrowed, keeping in mind the design must be substantially your own. If you cite your sources, worst case you may receive a reduced grade for borrowing too much. If you borrow, but do not cite, that is plagiarism and academic misconduct, and carries severe penalties as determined by the Faculty of Science.

As a guideline, consider the 20-minute rule. Talk with your colleagues and consult other sources (cite them please). Wait at least 20 minutes, then do your work to be sure that it is your own. Less than 20 minutes usually means that you are merely copying work from the original source.